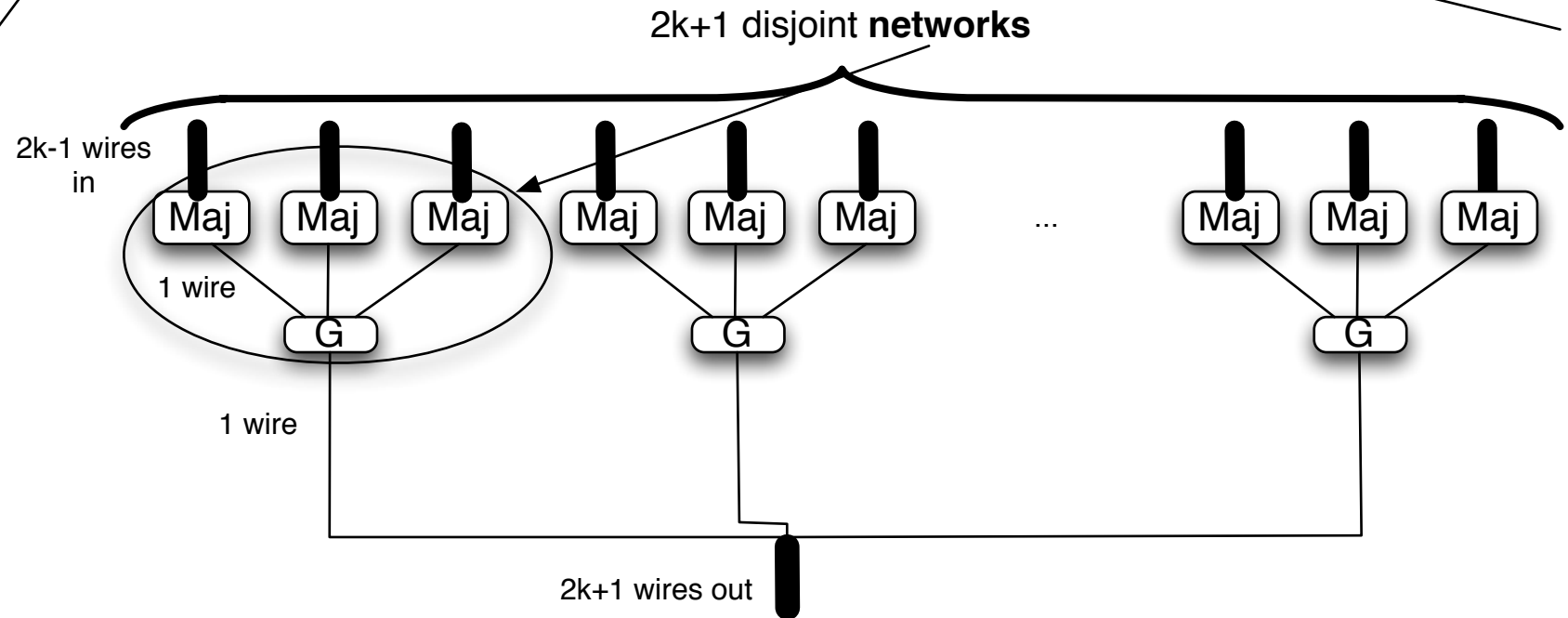


This is the **module** replacing each gate G at each level k:



Maj is a subcircuit that outputs the majority of its inputs. Each **network** requires $O(k)$ noiseless gates, so it can be built with $O(k \log k)$ noisy gates to ensure error probability less than 2ϵ . (See Part 1 in series)

Total gates in module = $O(k^2 \log k)$

Total gates in entire MUX = $\sum_{k=0}^r 2^{r-k} O(k^2 \log k) = O(2^r)$

We say a **network** errs if the wire leaving it has a different value than the wire leaving the corresponding gate, G, in the noiseless circuit. Say the entire **module** errs if a majority of the wires leaving it differ from wire leaving the corresponding G in the noiseless circuit

Each network has error probability no more than 2ϵ .
 So entire module has error prob. $\leq 2^{2k+1} (2\epsilon)^{k+1} = 4\epsilon(8\epsilon)^k$

So failure prob along any path is:

$$\leq \sum_{k=0}^r 4\epsilon(8\epsilon)^k \leq 4\epsilon / (1 - 8\epsilon) \leq 6\epsilon < 1/2$$

